ECE546 Milestone-2 Report

Team Members-

1. **Vaishnavi Avadhanam-200420812**
2. **Zachary Murray-200185195**
3. **Ramachandran Sekanipuram Srikanthan-200367158**

Overall Schematic for the SRAM-

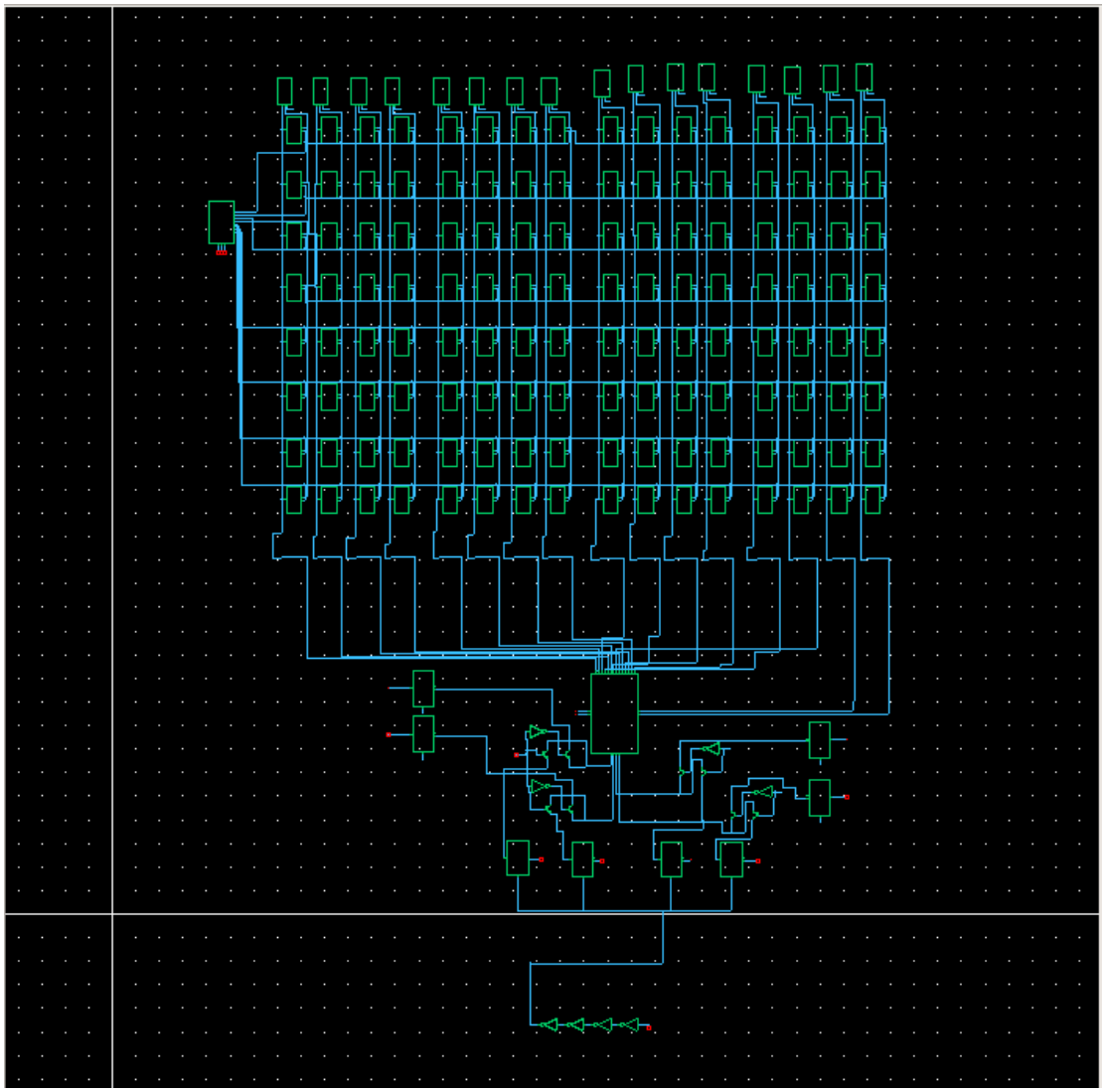

Waveform Results-

Bit Cell-

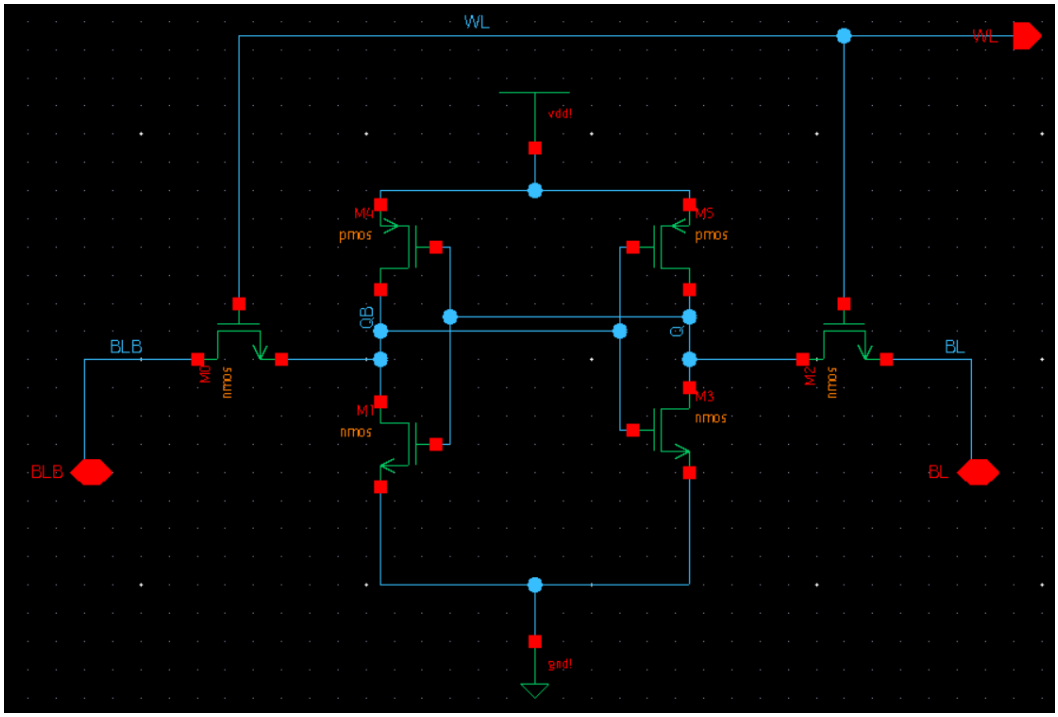
WL
WL
vdd!
M4
pmos
M5
pmos
QB
Q
BLB
M0
nmos
M1
nmos
M3
nmos
M2
nmos
BL
BLB
BL
gnd!

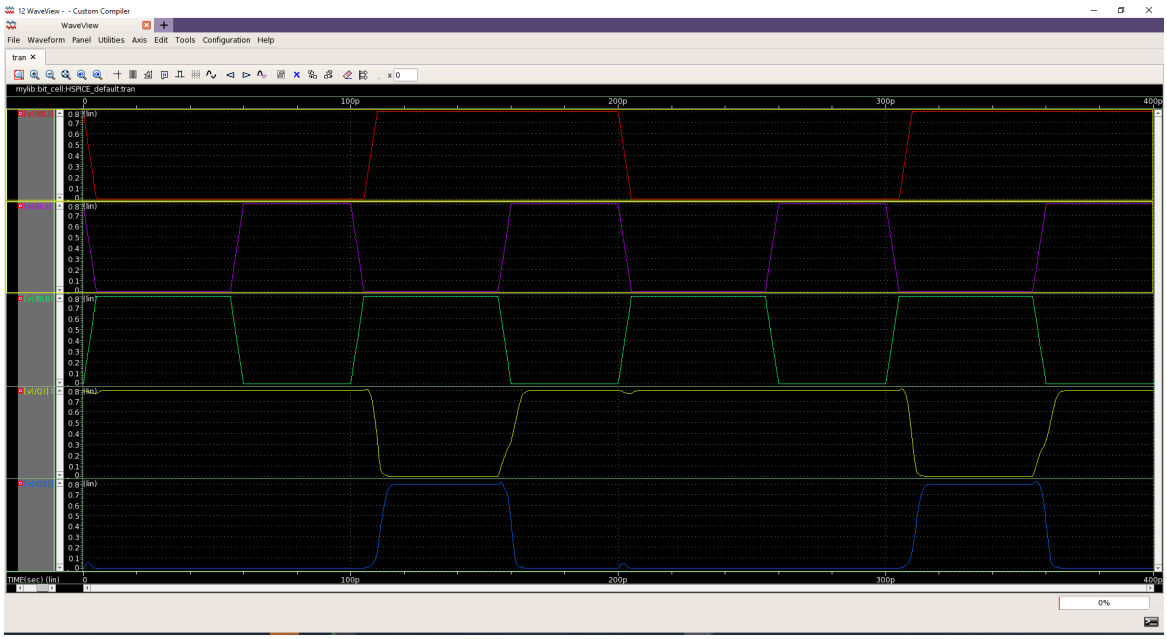
12 WaveView - - Custom Compiler
WaveView
File Waveform Panel Utilities Axis Edit Tools Configuration Help
tran
mylib bit_cell:HSPICE_default.tran
0
100p
200p
300p
400p
TIME(sec) (lin)

Bit-line-Conditioning-

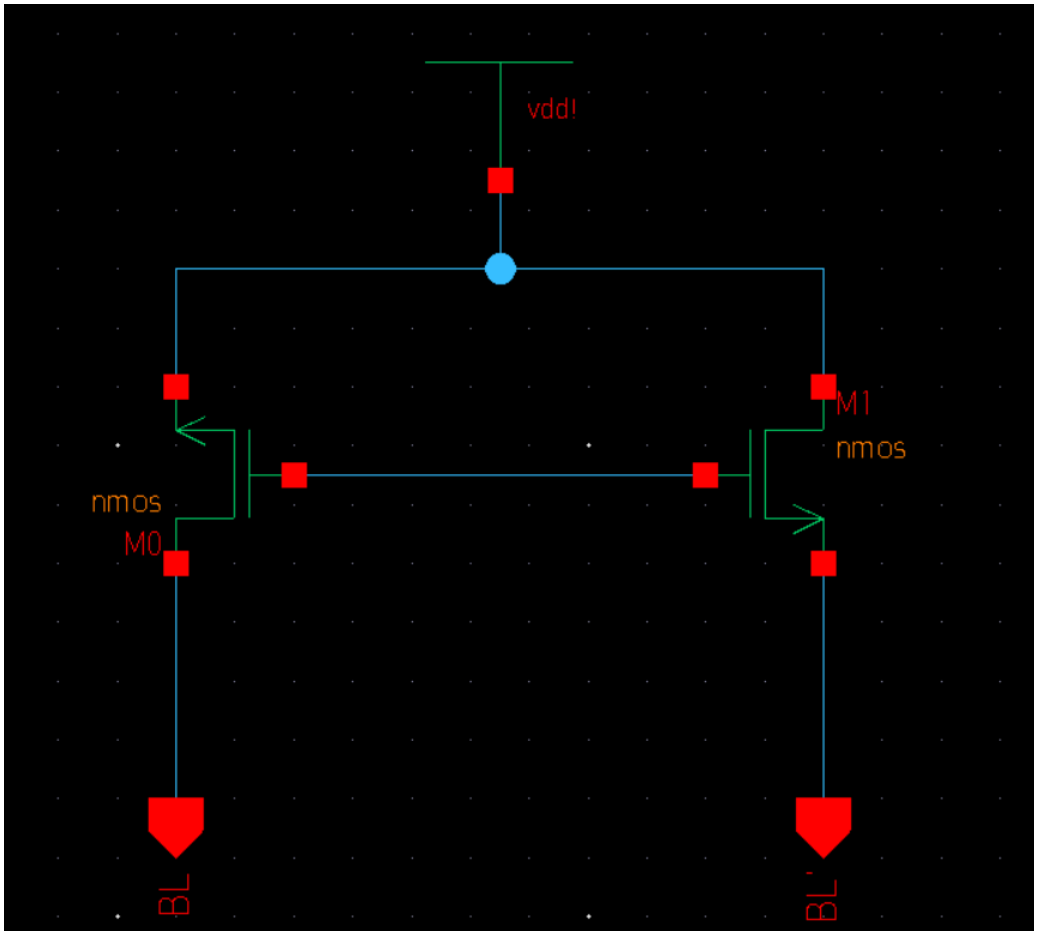

Row Decoder-

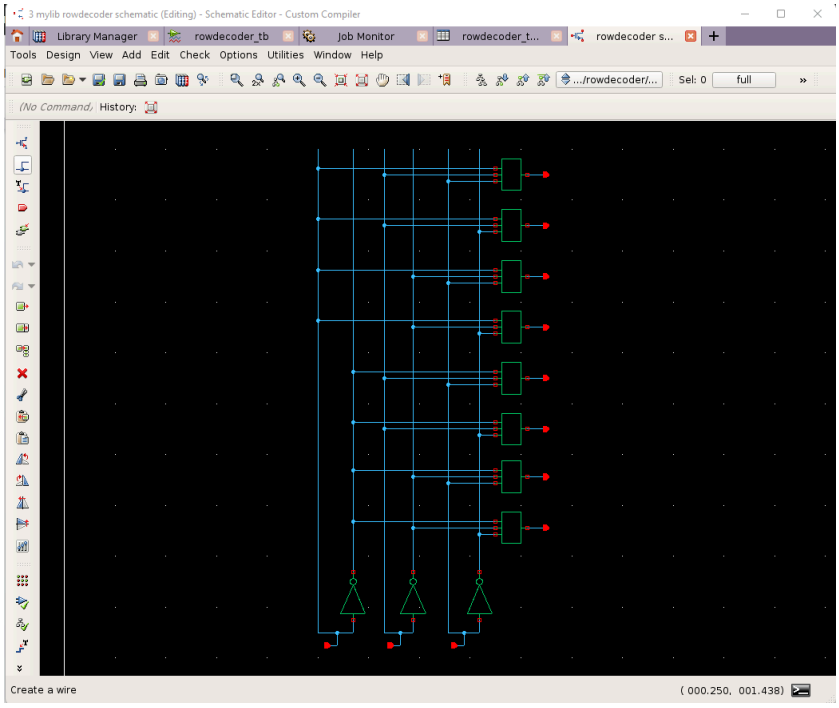
3 mylib rowdecoder schematic (Editing) - Schematic Editor - Custom Compiler
Library Manager
rowdecoder_tb
Job Monitor
rowdecoder_t...
rowdecoder s...
Tools Design View Add Edit Check Options Utilities Window Help
.../rowdecoder/...
Sel: 0
full
(No Command) History:
Create a wire
(000.250, 001.438)

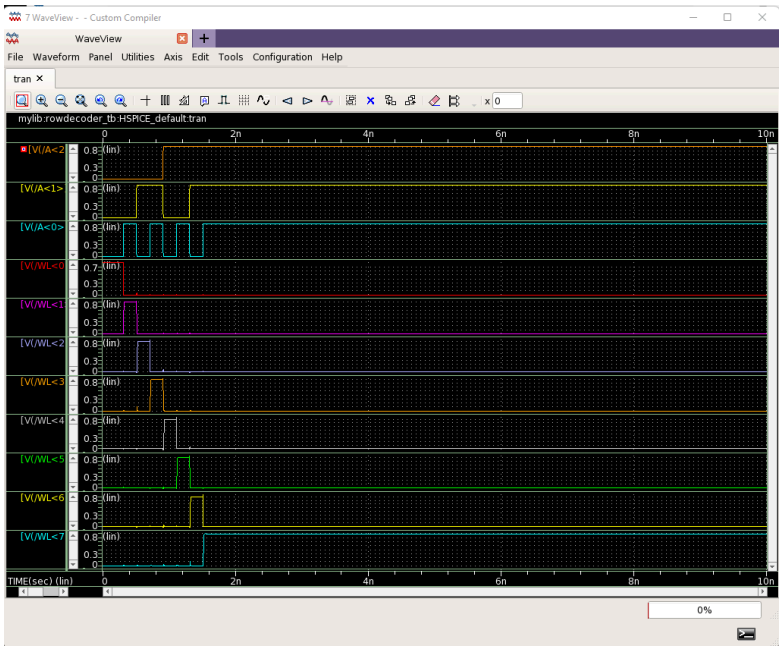
7 WaveView - - Custom Compiler
WaveView
File Waveform Panel Utilities Axis Edit Tools Configuration Help
tran
mylib:rowdecoder_tb:HSPICE_default:tran
[V(/A<2>
[V(/A<1>
[V(/A<0>
[V(/WL<0>
[V(/WL<1>
[V(/WL<2>
[V(/WL<3>
[V(/WL<4>
[V(/WL<5>
[V(/WL<6>
[V(/WL<7>
TIME(sec) (lin)
0
2n
4n
6n
8n
10n
0%

Column Decoder-

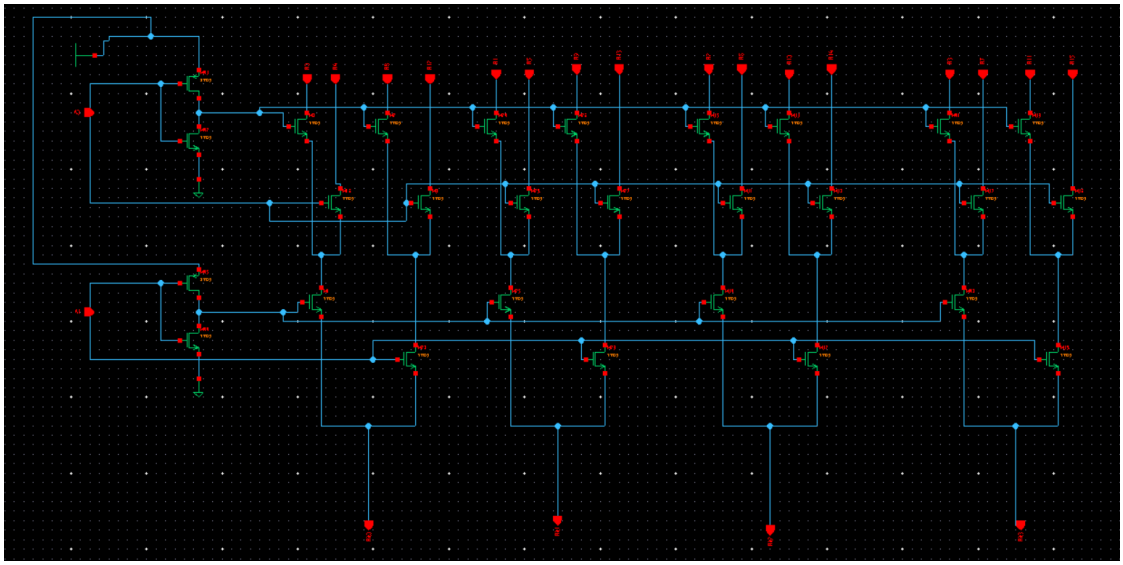
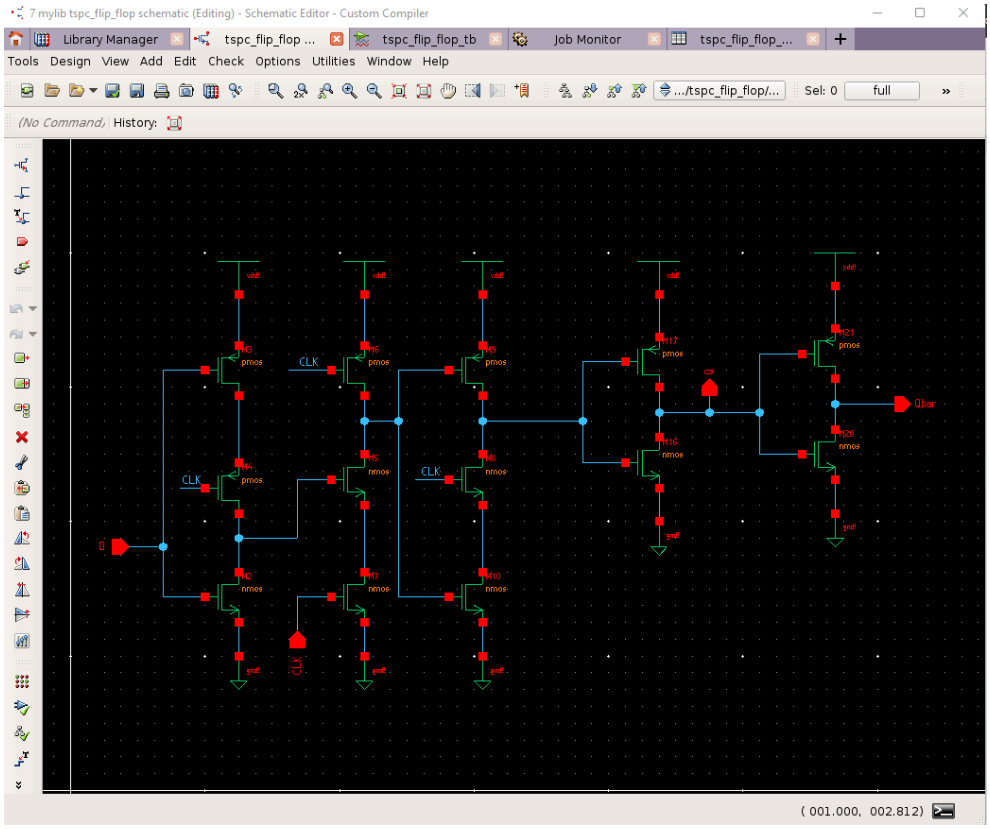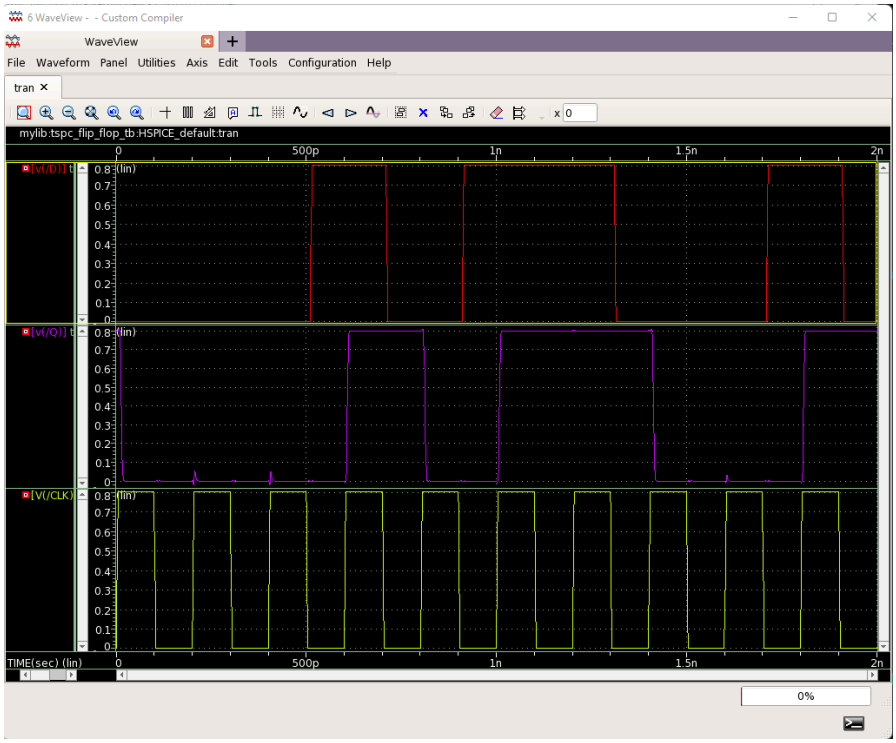
TSPC positive edge triggered Flip Flop-